

Lecture 8: Computer Arithmetic


- Last Time
 - Exceptions
 - Compiler's use of the ISA
 - Start of computer arithmetic
- Today
 - RISC vs. CISC + discussion
 - Carry-lookahead addition, shift, multiplication
 - Datapath organization

CISC vs RISC

- What is a RISC?
(Reduced Instruction Set Computer)
 - no firm definition
 - generally includes
 - general registers
 - fixed 3-address instruction format
 - strict load-store architecture
 - simple addressing modes
 - simple instructions
 - Examples
 - DEC Alpha
 - MIPS
 - Advantages
 - good compiler target
 - easy to implement/pipeline
- CISC (Complex Instruction-Set Computer)
 - $CISC \equiv \neg RISC$
 - may include
 - variable length instructions
 - memory-register instructions
 - complex addressing modes
 - complex instructions
 - CALLP, EDIT, ...
 - Examples
 - DEC VAX, IBM 370, x86
 - Advantages
 - better code density
 - legacy software


But What about Performance?

 - Critical Path of n-bit Ripple-carry adder is $n \cdot CP$




Design Trick: throw hardware at it


Carry Look Ahead (Design trick: peek)

 

Plumbing as Carry Lookahead Analogy

 


 Cascaded Carry Look-ahead (16-bit): Abstraction



Slide courtesy of D. Patterson

2nd level Carry, Propagate as Plumbing

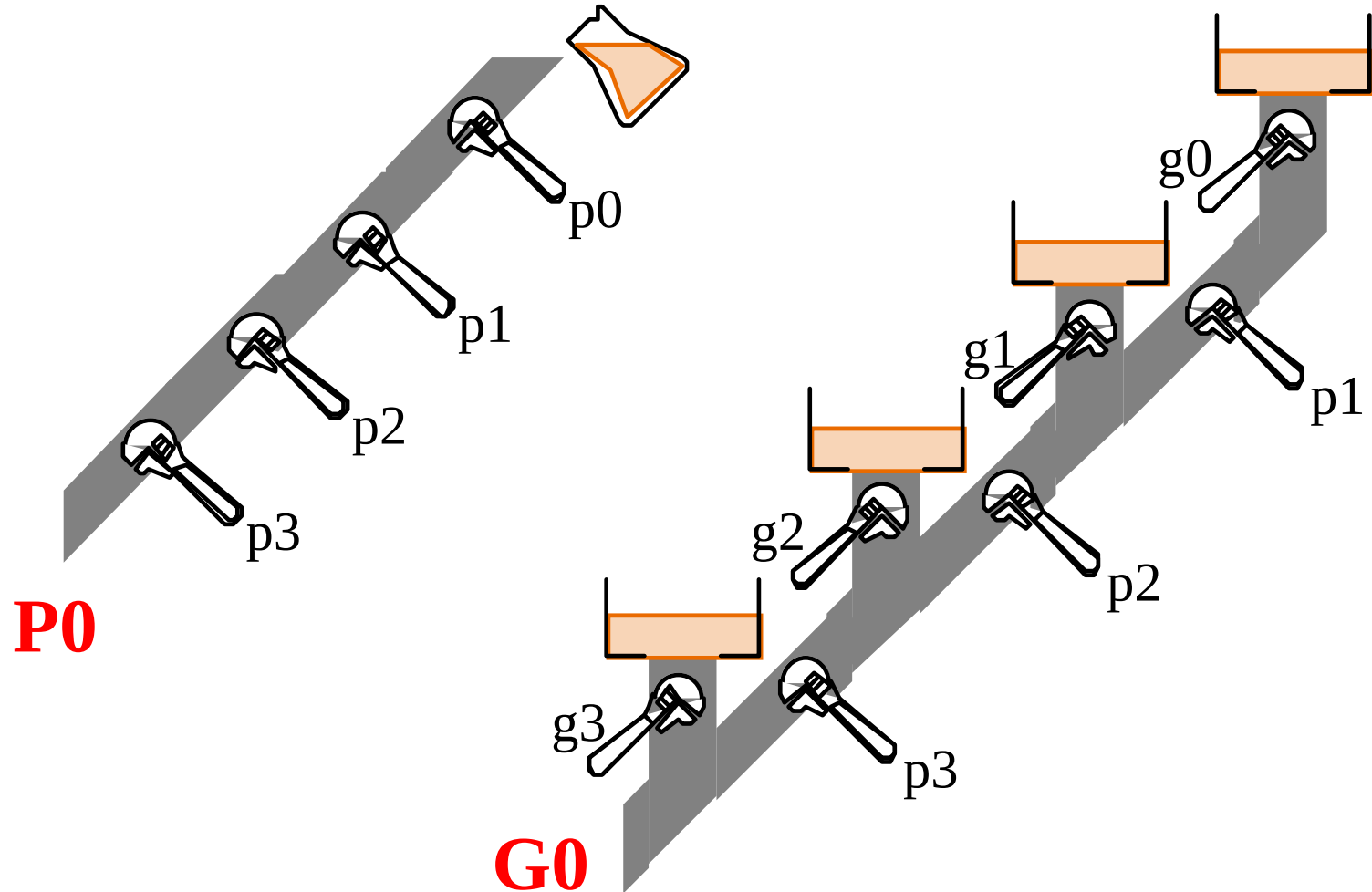


Delay Analysis


- 16-bit ripple carry adder
 - $T = 16 * T_{FA}$
 $= 16 * 2 \text{ gate delays} = 32 \text{ gate delays}$
- 16-bit carry lookahead adder
 - $T = T_{C4}$
 $= 2 + \max(P_i, G_i) = 2 + T_{G0}$
 $= 2 + 2 + \max(p_i, g_i)$
 $= 5 \text{ gate delays}$
 - Real designs use some nice transistor circuits for the carry lookahead chain
- In the limit - expand to full lookahead
 - $T = 2$ - but: a lot of logic, very wide fan-in gates
 - too costly

Design Trick: Guess

$$T(2n) = 2 * T(n)$$

 

$$T(2n) = T(n) + T(\text{mux})$$

 


Shifters

Two kinds:

logical-- value shifted in is always "0"



 
arithmetic-- on right shifts, sign extend



Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!


Combinational Shifter from MUXes

Basic Building Block

 


- What comes in the MSBs?
- How many levels for 32-bit shifter?
- What if we use 4-1 Muxes?

8-bit right shifter

 


 General Shift Right Scheme using 16 bit example



If added Right-to-left connections could support Rotate (not in MIPS but found in ISAs)

 Barrel Shifter - One transistor per switch



MULTIPLY (unsigned)

- Paper and pencil example (unsigned):

Multiplicand

1000

Multiplier

1001

1000

0000

0000


1000

01001000

Product


- m bits $\times$ n bits = $m+n$ bit product
- Binary makes it easy:
 - 0 $\Rightarrow$ place 0 (0 $\times$ multiplicand)
 - 1 $\Rightarrow$ place a copy (1 $\times$ multiplicand)
- 4 versions of multiply hardware & algorithm:
 - successive refinement

Unsigned Combinational Multiplier

 

- Stage i accumulates $A * 2^i$ if $B_i == 1$
- Q: How much hardware for 32 bit multiplier? Critical path?


How does it work?

 

- at each stage shift A left ($\times 2$)
- use next bit of B to determine whether to add in shifted multiplicand
- accumulate $2n$ bit partial product at each stage

Unsigned shift-add multiplier (version 1)

 - 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg




Multiplier = datapath + control

Observations on Multiply Version 1


- 1 clock per cycle => - 100 clocks per multiply
 - Ratio of multiply to add 5:1 to 100:1
- 1/2 bits in multiplicand always 0
 - => 64-bit adder is wasted
- 0's inserted in left of multiplicand as shifted
 - => least significant bits of product never changed once formed
- Instead of shifting multiplicand to left, shift product to right?

MULTIPLY HARDWARE Version 2

 - 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg




What's going on?

 

- Multiplicand stay's still and product moves right

MULTIPLY HARDWARE Version 3

 - Still wasting some storage space
 - Bits of multiplier used one-by-one, can overlap with product
- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



Observations on Multiplication

- Can speed up algorithm by doing 2 bits at a time, instead of just one
 - How????
 - See Booth encoding strategy in chapter 4
- Multiplication algorithm is still slow
 - Each step is doing a full carry-propagate add
 - Can use carry save adders instead
 - Build a Wallace tree to combine the partial products
 - Single carry-propagate add instead
- Division algorithm is very similar to multiplication
 - See section 4.7

Summary

- Add/Shift/Multiply
- Next Time
 - Pipelining basics
 - Data/Control Hazards - up close and personal
 - Pipelining Multicycle instructions
- Reading assignment - P&H 4.8-4.12 (skim)
P&H Chapter 5 (skim)