

Lecture 9: Datapaths and Pipelining


- Logistics
 - Homework #2 due
 - Homework #3 will be posted later today – due next Thur.
- Last Time
 - RISC vs. CISC + discussion
 - Carry-lookahead addition, shift, multiplication
- Today
 - Datapath organization
 - Introduction to pipelining

Observations on Multiplication

- Can speed up algorithm by doing 2 bits at a time, instead of just one
 - How????
 - See Booth encoding strategy in chapter 4
- Multiplication algorithm is still slow
 - Each step is doing a full carry-propagate add
 - Can use carry save adders instead
 - Build circuit to combine the partial products
- Division algorithm is very similar to multiplication
 - See section 4.7

Instruction Execution

 - 5 basic steps
 - fetch instruction (F)
 - decode instruction/read registers (R)
 - execute (X)
 - access memory (M)
 - store result (W)



Change to paper lecture media...
[see PDF file for Part 2 of lecture]


(Datapath Microarchitecture)

Pipelining

Optimizing the Processor

No shared resources


No hidden state

 

Interestingly – we can get rid of most of the datapath flip-flops
“Single-cycle execution”

Datapath Timing

 
Instruction execution time = ? Clock frequency = ?



Can Re-insert Datapath Flip-Flops




“Multicycle Execution”

 Instruction execution time = ? Clock frequency = ?




Pipelining is Natural!

   - Laundry Example
- Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, and fold
- Washer takes 30 minutes
- Dryer takes 30 minutes
- “Folder” takes 30 minutes
- “Stasher” takes 30 minutes to put clothes into drawers




Sequential Laundry

 

- Sequential laundry takes 8 hours for 4 loads
- If they learned pipelining, how long would laundry take?


Pipelined Laundry: Start work ASAP

 

- Pipelined laundry takes 3.5 hours for 4 loads!


Sequential Logic

 - State elements
 - flip flops, registers, memories
- Common clock
- Separated by combination logic
- Feedback allowed




Clocking and Clocked Elements

 - Typical Clock
 - 1Hz = 1 cycle per second




- Transparent Latch

 


CLK=0, Q=oldQ
CLK=1, Q=D

- Edge Triggered Flip-Flop

 


Storage Element's Timing Model

 

- Setup Time: Input must be stable BEFORE the trigger clock edge
- Hold Time: Input must REMAIN stable after the trigger clock edge
- Clock-to-Q time:
 - Output cannot change instantaneously at the trigger clock edge
 - Similar to delay in logic gates, two components:
 - Internal Clock-to-Q
 - Load dependent Clock-to-Q

Clocking Methodology

 


- All storage elements are clocked by the same clock edge
- The combination logic block's:
 - Inputs are updated at each clock tick
 - All outputs **MUST** be stable before the next clock tick

Can Re-insert Datapath Flip-Flops

“Multicycle Execution”

 Instruction execution time = ? Clock frequency = ?



Summary

- Datapath organization
- Control: hardwired and microcode
- Datapath optimization
- Pipelining introduction

- Next Time
 - Pipeline hazards

- Reading assignment – P&H 6.1-6.2